


VHDL Based Digital Circuits Design

**Digital Systems Course
2nd Year Students**

**Tanta University
Faculty of Engineering
Computer & Control Engineering Department
2014-2015**

We introduce here some examples of VHDL based digital circuits design for Lab work.

4-Bit Adder/Subtractor

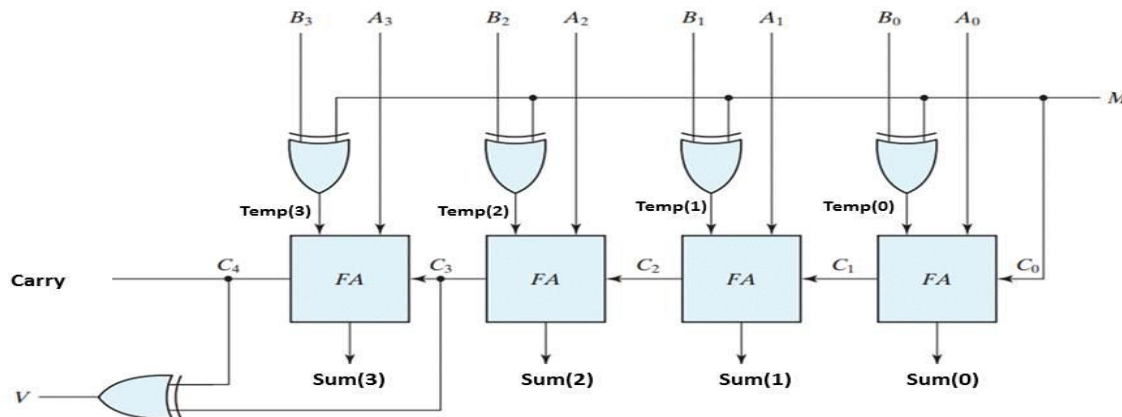

--XOR gate VHDL code

Library ieee;

Use ieee.std_logic_1164.all;

Entity xor_gate is

Port(A, B: in std_logic;

F: out std_logic);

End xor_gate;

Architecture xor_behav of xor_gate is

Begin

F <= A xor B;

End xor_behav;

--Full adder VHDL code

Library ieee;

Use ieee.std_logic_1164.all;

Entity FA is

Port(X, Y, Cin: in std_logic;

Sum, Cout: out std_logic);

End FA;

Architecture FA_behav of FA is

Begin

Sum <= (X xor Y) xor Cin;

```
Cout <= (X and Y) or( (X xor Y) and Cin);  
End FA_behav;
```

--Top level 4-bit AdderSubtractor

```
Library ieee;  
Use ieee.std_logic_1164.all;
```

```
Entity Addsub is  
Port( M: in std_logic;  
      A, B: in std_logic_vector(3 downto 0);  
      Sum: out std_logic_vector(3 downto 0);  
      Carry, V: out std_logic);  
End Addsub;
```

```
Architecture Addsub_Sruct of Addsub is  
Component xor_gate is  
Port( A, B: in std_logic;  
      F: out std_logic);  
End component;  
Component FA is  
Port( X, Y,Cin: in std_logic;  
      Sum,Cout: out std_logic);  
End component;
```

```
Signal C :std_logic_vector(4 downto 1);  
Signal temp: std_logic_vector(3 downto 0);
```

```
Begin
```

```
XG1: xor_gate port map (M, B(0),temp(0));  
XG2: xor_gate port map (M, B(1),temp(1));  
XG3:xor_gate port map (M, B(2),temp(2));  
XG4: xor_gate port map (M, B(3),temp(3));
```

```
FA0: FA port map (A(0), temp(0), M, Sum(0),C(1));  
FA1: FA port map (A(1), temp(1), C(1), Sum(1),C(2));  
FA2: FA port map (A(2), temp(2), C(2), Sum(2),C(3));  
FA3: FA port map (A(3), temp(3), C(3), Sum(3),C(4));
```

```
V <= C(3) xor C(4);  
Carry <= C4;
```

```
End Addsub_Struct;
```

4-to 1 Mux using If statement

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY mux4_1 IS
    PORT (s0          : IN  STD_LOGIC;
          s1          : IN  STD_LOGIC;
          in0         : IN  STD_LOGIC;
          in1         : IN  STD_LOGIC;
          in2         : IN  STD_LOGIC;
          in3         : IN  STD_LOGIC;
          output      : OUT STD_LOGIC
    );
END mux4_1;

ARCHITECTURE if_example OF mux4_1 IS

BEGIN

mux:PROCESS(s0, s1, in0, in1, in2, in3)
BEGIN

    IF      (s0='0' AND s1='0') THEN
        output <= in0;
    ELSIF   (s0='1' AND s1='0') THEN
        output <= in1;
    ELSIF   (s0='0' AND s1='1') THEN
        output <= in2;
    ELSIF   (s0='1' AND s1='1') THEN
        output <= in3;
    ELSE    -- (s0 or s1 are not 0 or 1)
        output <= 'X';
    END IF;

END PROCESS mux;

END if_example;
```

4-to1 Mux using case statement

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;      -- Package declaration.

ENTITY mux4_1 IS
    PORT (s0          : IN  STD_LOGIC;
          s1          : IN  STD_LOGIC;
          in0         : IN  STD_LOGIC;
          in1         : IN  STD_LOGIC;
          in2         : IN  STD_LOGIC;
          in3         : IN  STD_LOGIC;
          output      : OUT STD_LOGIC
    );
END mux4_1;
```

```
ARCHITECTURE case_example OF mux4_1 IS

BEGIN

mux:PROCESS(s0, s1, in0, in1, in2, in3)
    VARIABLE sel : STD_LOGIC_VECTOR(1 DOWNT0 0);
BEGIN
    sel := s1 & s0;    -- concatenate s1 and s0

    CASE sel IS
        WHEN "00" => output <= in0;
        WHEN "01" => output <= in1;
        WHEN "10" => output <= in2;
        WHEN "11" => output <= in3;
        WHEN OTHERS => output <= 'X';
    END CASE;

END PROCESS mux;

END case_example;
```

2-to 1 Mux using (with –select) statement

```
library ieee;
    use ieee.std_logic_1164.all;

entity mux_using_with is
    port (
        din_0    :in  std_logic; -- Mux first input
        din_1    :in  std_logic; -- Mux Second input
        sel       :in  std_logic; -- Select input
        mux_out   :out std_logic  -- Mux output
    );
end entity;

architecture behavior of mux_using_with is

begin
    with (sel) select
        mux_out <= din_0 when '0',
                  din_1 when others;

end architecture;
```

16-to 4 Encoder - Using if-else Statement

```
-----
-- Design Name : encoder_using_if
-- File Name    : encoder_using_if.vhd
-----

library ieee;
    use ieee.std_logic_1164.all;
```

```
entity encoder_using_if is
    port (
        enable      :in  std_logic;           -- Enable for the encoder
        encoder_in   :in  std_logic_vector (15 downto 0); -- 16-bit Input
        binary_out   :out std_logic_vector (3 downto 0)   -- 4 bit binary
Output
    );
end entity;
```

architecture behavior of encoder_using_if is

```
begin
    process (enable, encoder_in) begin
        binary_out <= "0000";
        if (enable = '1') then
            if (encoder_in = X"0002") then binary_out <= "0001"; end if;
            if (encoder_in = X"0004") then binary_out <= "0010"; end if;
            if (encoder_in = X"0008") then binary_out <= "0011"; end if;
            if (encoder_in = X"0010") then binary_out <= "0100"; end if;
            if (encoder_in = X"0020") then binary_out <= "0101"; end if;
            if (encoder_in = X"0040") then binary_out <= "0110"; end if;
            if (encoder_in = X"0080") then binary_out <= "0111"; end if;
            if (encoder_in = X"0100") then binary_out <= "1000"; end if;
            if (encoder_in = X"0200") then binary_out <= "1001"; end if;
            if (encoder_in = X"0400") then binary_out <= "1010"; end if;
            if (encoder_in = X"0800") then binary_out <= "1011"; end if;
            if (encoder_in = X"1000") then binary_out <= "1100"; end if;
            if (encoder_in = X"2000") then binary_out <= "1101"; end if;
            if (encoder_in = X"4000") then binary_out <= "1110"; end if;
            if (encoder_in = X"8000") then binary_out <= "1111"; end if;
        end if;
    end process;
end architecture;
```

16 to 4 Encoder - Using case Statement

```
-- Design Name : encoder_using_case
-- File Name   : encoder_using_case.vhd
-- Function    : Encoder using Case
-----
library ieee;
    use ieee.std_logic_1164.all;

entity encoder_using_case is
    port (
        enable      :in  std_logic;           -- Enable for the encoder
        encoder_in   :in  std_logic_vector (15 downto 0); -- 16-bit Input
        binary_out   :out std_logic_vector (3 downto 0)   -- 4 bit binary
Output
    );
end entity;
```

```
architecture behavior of encoder_using_case is
begin
    process (enable, encoder_in) begin
        if (enable = '1') then
            case (encoder_in) is
                when X"0002" => binary_out <= "0001";
                when X"0004" => binary_out <= "0010";
                when X"0008" => binary_out <= "0011";
                when X"0010" => binary_out <= "0100";
                when X"0020" => binary_out <= "0101";
                when X"0040" => binary_out <= "0110";
                when X"0080" => binary_out <= "0111";
                when X"0100" => binary_out <= "1000";
                when X"0200" => binary_out <= "1001";
                when X"0400" => binary_out <= "1010";
                when X"0800" => binary_out <= "1011";
                when X"1000" => binary_out <= "1100";
                when X"2000" => binary_out <= "1101";
                when X"4000" => binary_out <= "1110";
                when X"8000" => binary_out <= "1111";
                when others => binary_out <= "0000";
            end case;
        end if;
    end process;
end architecture;
```

Priority-Encoder - Using if-else Statement

```
-----
-- Design Name : pri_encoder_using_if
-- File Name   : pri_encoder_using_if.vhd
-- Function    : Pri Encoder using If
-----

library ieee;
    use ieee.std_logic_1164.all;

entity pri_encoder_using_if is
    port (
        enable      :in  std_logic;           -- Enable for the encoder
        encoder_in  :in  std_logic_vector (15 downto 0); -- 16-bit Input
        binary_out  :out std_logic_vector (3 downto 0)  -- 4 bit binary
    );
end entity;

architecture behavior of pri_encoder_using_if is
begin
    process (enable, encoder_in) begin
        binary_out <= "0000";
        if (enable = '1') then
```

```
        if (encoder_in = "XXXXXXXXXXXXX10") then
            binary_out <= "0001";
        elsif (encoder_in = "XXXXXXXXXXXXX100") then
            binary_out <= "0010";
        elsif (encoder_in = "XXXXXXXXXXXXX1000") then
            binary_out <= "0011";
        elsif (encoder_in = "XXXXXXXXXXXXX10000") then
            binary_out <= "0100";
        elsif (encoder_in = "XXXXXXXXXXXXX100000") then
            binary_out <= "0101";
        elsif (encoder_in = "XXXXXXXXXXXXX1000000") then
            binary_out <= "0110";
        elsif (encoder_in = "XXXXXXXXXXXXX10000000") then
            binary_out <= "0111";
        elsif (encoder_in = "XXXXXXXXXXXXX100000000") then
            binary_out <= "1000";
        elsif (encoder_in = "XXXXXXXXXXXXX1000000000") then
            binary_out <= "1001";
        elsif (encoder_in = "XXXXXXXXXXXXX10000000000") then
            binary_out <= "1010";
        elsif (encoder_in = "XXXXX100000000000") then
            binary_out <= "1011";
        elsif (encoder_in = "XXX1000000000000") then
            binary_out <= "1100";
        elsif (encoder_in = "XX10000000000000") then
            binary_out <= "1101";
        elsif (encoder_in = "X100000000000000") then
            binary_out <= "1110";
        else
            binary_out <= "1111";
        end if;
    end if;
end process;
end architecture;
```

Priority Encoder - Using when Statement

```
-----
-- Design Name : pri_encoder_using_when
-- File Name    : pri_encoder_using_when.vhd
-- Function     : Pri Encoder using when-else
-----

library ieee;
    use ieee.std_logic_1164.all;

entity pri_encoder_using_when is
    port (
        enable      :in  std_logic;           -- Enable for the encoder
        encoder_in   :in  std_logic_vector (15 downto 0); -- 16-bit Input
        binary_out   :out std_logic_vector (3 downto 0)    -- 4 bit binary
    );
end entity;

architecture behavior of pri_encoder_using_when is
```



```
begin
    binary_out <= "0000" when (enable = '0') else
        "0000" when (encoder_in = "XXXXXXXXXXXXXXXXX1") else
        "0001" when (encoder_in = "XXXXXXXXXXXXXXXXX10") else
        "0010" when (encoder_in = "XXXXXXXXXXXXXXXXX100") else
        "0011" when (encoder_in = "XXXXXXXXXXXXXXXXX1000") else
        "0100" when (encoder_in = "XXXXXXXXXXXXXXXXX10000") else
        "0101" when (encoder_in = "XXXXXXXXXXXXXXXXX100000") else
        "0110" when (encoder_in = "XXXXXXXXXXXXX1000000") else
        "0111" when (encoder_in = "XXXXXXXXXXXXX10000000") else
        "1000" when (encoder_in = "XXXXXXXXX1000000000") else
        "1001" when (encoder_in = "XXXXXXXXX10000000000") else
        "1010" when (encoder_in = "XXXXXX100000000000") else
        "1011" when (encoder_in = "XXXXX1000000000000") else
        "1100" when (encoder_in = "XXX100000000000000") else
        "1101" when (encoder_in = "XX1000000000000000") else
        "1110" when (encoder_in = "X10000000000000000") else
        "1111";

end architecture;
```

4 to 16 Decoder - Using case Statement

```
library ieee;
    use ieee.std_logic_1164.all;

entity decoder_using_case is
    port (
        enable      :in  std_logic;           -- Enable for the decoder
        binary_in   :in  std_logic_vector (3 downto 0); -- 4-bit Input
        decoder_out  :out std_logic_vector (15 downto 0) -- 16-bit Output
    );
end entity;

architecture behavior of decoder_using_case is

begin
    process (enable, binary_in) begin
        decoder_out <= X"0000";
        if (enable = '1') then
            case (binary_in) is
                when X"0"   => decoder_out <= X"0001";
                when X"1"   => decoder_out <= X"0002";
                when X"2"   => decoder_out <= X"0004";
                when X"3"   => decoder_out <= X"0008";
                when X"4"   => decoder_out <= X"0010";
                when X"5"   => decoder_out <= X"0020";
                when X"6"   => decoder_out <= X"0040";
                when X"7"   => decoder_out <= X"0080";
                when X"8"   => decoder_out <= X"0100";
                when X"9"   => decoder_out <= X"0200";
                when X"A"   => decoder_out <= X"0400";
                when X"B"   => decoder_out <= X"0800";
                when X"C"   => decoder_out <= X"1000";
            end case;
        end if;
    end process;

end architecture;
```

```
        when X"D"    => decoder_out <= X"2000";
        when X"E"    => decoder_out <= X"4000";
        when X"F"    => decoder_out <= X"8000";
        when others => decoder_out <= X"0000";
    end case;
end if;
end process;
end architecture;
```

4 to 16 Decoder using (with-select) statement

```
-----
-- Design Name : decoder_using_with
-- File Name   : decoder_using_with.vhd
-- Function    : decoder using with-select
-----

library ieee;
    use ieee.std_logic_1164.all;

entity decoder_using_select is
    port (
        enable      :in  std_logic;           -- Enable for the decoder
        binary_in   :in  std_logic_vector (3 downto 0); -- 4-bit input
        decoder_out  :out std_logic_vector (15 downto 0) -- 16-bit output
    );
end entity;

architecture behavior of decoder_using_select is

begin
    with (binary_in) select
        decoder_out <= X"0001" when X"0",
                        X"0002" when X"1",
                        X"0004" when X"2",
                        X"0008" when X"3",
                        X"0010" when X"4",
                        X"0020" when X"5",
                        X"0040" when X"6",
                        X"0080" when X"7",
                        X"0100" when X"8",
                        X"0200" when X"9",
                        X"0400" when X"A",
                        X"0800" when X"B",
                        X"1000" when X"C",
                        X"2000" when X"D",
                        X"4000" when X"E",
                        X"8000" when X"F",
                        X"0000" when others;

end architecture;
```

A Flip-flop is the basic element which is used to store information of one bit. Flip-flops have their content change either at the rising or falling edge of the enable signal(usually the controlling clock signal).


There are basically four main types of flip-flops:

1. SR Flip-flop
2. D Flip-flop
3. JK Flip-flop
4. T Flip-flop.

 1. SR FLIP-FLOP VHDL Code:

A SR flip flop used in digital electronics will provide the results in a similar manner to the JK flip flop and this is the reason why the vhdl codes for these two flipflops are similar in nature.

Given below is a behavioral approach of writing the code for a SR Flip-flop.



```
library ieee;
use ieee. std_logic_1164.all;
use ieee. std_logic_arith.all;
use ieee. std_logic_unsigned.all;
```

```
entity SR-FF is
PORT( S,R,CLOCK,CLR,PRESET: in std_logic;
      Q, QBAR: out std_logic);
end SR-FF;
```

Architecture behavioral of SR-FF is

```
begin
P1: PROCESS(CLOCK,CLR,PRESET)
variable x: std_logic;
begin
if(CLR='0') then
x:='0';

elsif(PRESET='0')then
x:='1';

elsif(CLOCK='1' and CLOCK'EVENT) then

if(S='0' and R='0')then
x:=x;
elsif(S='1' and R='1')then
x:='Z';

elsif(S='0' and R='1')then
x:='0';

else
x:='1';


end if;
end if;

Q<=x;
QBAR<=not x;
end PROCESS;
end behavioral;
```

 2. D FLIP-FLOP VHDL Code:

A D flip flop or Delay flip flop gives the same output as the input provided and thus the vhdl code is much simpler.

Given below is a behavioral approach of writing the vhdl code for a D Flip-flop.



```
library ieee;
use ieee. std_logic_1164.all;
use ieee. std_logic_arith.all;
use ieee. std_logic_unsigned.all;

entity D-FF is
PORT( D,CLK,RST: in std_logic;
      Q: out std_logic);
end D-FF;

architecture behavioral of D-FF is

begin
P1: process(RST,CLK)


begin

if(RST='1')then
Q<='0';

elseif(CLK='1' and CLK'EVENT) then
Q<=D;
end if; end process;
end behavioral;
```

 3. JK FLIP-FLOP VHDL Code:

Given below is a behavioral approach of writing the code for a JK Flip-flop.



```
library ieee;
use ieee. std_logic_1164.all;
use ieee. std_logic_arith.all;
use ieee. std_logic_unsigned.all;

entity JK-FF is
PORT( J,K,CLK,PRST,CLR: in std_logic;
      Q, QB: out std_logic);
end JK-FF;
```

```
Architecture behavioral of JK-FF is
begin
P1: PROCESS(CLK,CLR,PRST)
variable x: std_logic;
begin
if(CLR='0') then
x:='0';


elsif(PRST='0')then
```

```
x:='1';  
  
elsif(CLK='1' and CLK'EVENT) then  
  if(J='0' and K='0')then  
    x:=x;  
  elsif(J='1' and K='1')then  
    x:= not x;  
  
  elsif(J='0' and K='1')then  
    x:='0';  
  else  
    x:='1';  
  
  end if;  
end if;  
Q<=x;  
QB<=not x;  
end PROCESS;  
end behavioral;
```

 4. T FLIP-FLOP VHDL Code:

The T in a t flip flop stands for toggle and this is exactly what this digital component does. It simply toggles the value of a particular input. A basic not gate will solve the problem in the vhd code for this element.

Given below is a behavioral approach of writing the code for a T Flip-flop.



```
library ieee;
use ieee. std_logic_1164.all;
use ieee. std_logic_arith.all;
use ieee. std_logic_unsigned.all;

entity T-FF is

PORT( T,CLK,PRST,RST: in std_logic;
      Q: out std_logic);

end T-FF;

architecture behavioral of T-FF is

begin
P1: process(CLK,PRST,RST)

variable x: std_logic;

begin

if(RST='0') then

x:='0';

elsif(RST='1' and PRST='0') then

x:='1';

elsif(CLK='1' and CLK'EVENT) then

if(T='1')then

x:= not x;

end if;
end if;

Q<=x;

end process;
end behavioral;
```

Regular D latch(register)

```
library ieee;
use ieee.std_logic_1164.all;

entity dlatch_reset is
    port (
        data  :in  std_logic; -- Data input
        en    :in  std_logic; -- Enable input
        reset :in  std_logic; -- Reset input
        q     :out std_logic  -- Q output
    );
end entity;

architecture rtl of dlatch_reset is
begin
    process (en, reset, data) begin
        if (reset = '0') then
            q <= '0';
        elsif (en = '1') then
            q <= data;
        else
            null;
        end if;
    end process;
end architecture;
```

8-bit Parallel to Serial converter

```
-- Description
-- Implements a simple 8-bit parallel to serial converter in VHDL.

library ieee;
use ieee.std_logic_1164.all;

entity PAR2SER is
    port (DIN : in std_logic_vector (7 downto 0); -- input register
          MODE : in std_logic_vector (1 downto 0); -- mode selection
          CLK, RESET : in std_logic; -- clock and reset
          SDOUT : out std_logic); -- output data
end PAR2SER;

-- purpose: Implement main architecture of PAR2SER

architecture BEHAVIOR of PAR2SER is

    signal IDATA : std_logic_vector(7 downto 0); -- internal data
```

```
begin -- BEHAVIOR

-- purpose: Main process
process (CLK, RESET)
begin -- process
-- activities triggered by asynchronous reset (active high)

if RESET = '1' then
SDOUT <= '0';
IDATA <= "00000000";
-- activities triggered by rising edge of clock
elsif CLK'event and CLK = '1' then

case MODE is
when "00" => -- no operation
null;
when "01" => -- load operation
IDATA <= DIN;
when "10" => -- shift left
SDOUT <= IDATA(7);
for mloop in 6 downto 0 loop
IDATA(mloop+1) <= IDATA(mloop);
end loop; -- mloop
when others => -- no operation otherwise
null;
end case;

end if;

end process;

end BEHAVIOR;
```

BCD to 7-Seg Decoder

```
library IEEE;

use IEEE.std_logic_1164.all;

use IEEE.std_logic_unsigned.all;

entity DISPLAY_DECODER is

port ( VALUE : in bit_vector(3 downto 0); -- Bit 3 is MSB

ZERO_BLANK : in bit;

DISPLAY : out bit_vector(6 downto 0); -- 7 bit signal

ZERO_BLANK_OUT : out bit);
```

```
end DISPLAY_DECODER;
```

architecture BEHAVIOUR of DISPLAY_DECODER is

```
begin
```

```
process (VALUE, ZERO_BLANK)    -- sensitivity list
```

```
begin
```

```
case VALUE is -- case-when statement described how decode is
```

```
-- driven based on the value of the input.
```

```
when "0000" => if ZERO_BLANK='1' then
```

```
    DISPLAY <= "0000000";
```

```
    ZERO_BLANK_OUT <= '1';
```

```
else
```

```
    DISPLAY <= "1111110";
```

```
end if;
```

```
when "0001" => DISPLAY <= "0110000";
```

```
when "0010" => DISPLAY <= "1101101";
```

```
when "0011" => DISPLAY <= "1111001";
```

```
when "0100" => DISPLAY <= "0110011";
```

```
when "0101" => DISPLAY <= "1011011";
```

```
when "0110" => DISPLAY <= "1011111";
```

```
when "0111" => DISPLAY <= "1110000";
```

```
when "1000" => DISPLAY <= "1111111";
```

```
when OTHERS => DISPLAY <= "1001111"; -- when others, an error is specified
```

```
end case;
```

```
end process;
```

```
end BEHAVIOUR;
```

Test bench

```
library IEEE;
```

```
use IEEE.std_logic_1164.all;
```

```
use IEEE.std_logic_unsigned.all;
```

```
entity DISPLAY_DECODER_TB is
```

```
end DISPLAY_DECODER_TB;
```

```
architecture ARC_DISPLAY_DECODER_TB of DISPLAY_DECODER_TB is
```

```
signal VALUE      : bit_vector(3 downto 0);
```

```
signal ZERO_BLANK  : bit;
```

```
signal DISPLAY     : bit_vector(6 downto 0);
```

```
signal ZERO_BLANK_OUT : bit;
```

```
component DISPLAY_DECODER
```

```
port ( VALUE      : in bit_vector(3 downto 0);
```

```
ZERO_BLANK      : in bit;
```

```
DISPLAY         : out bit_vector(6 downto 0);
```

```
ZERO_BLANK_OUT  : out bit);
```

```
end component;
```

```
begin
```

```
INPUT_VALUES: process
```

```
begin
```

```
ZERO_BLANK <= '1';
```

```
VALUE <= "0000";
```

```
wait for 5 ns;
```

```
ZERO_BLANK    <= '0';

VALUE         <= "0000";

wait for 7 ns;

ZERO_BLANK <= '1';

VALUE <= "0010";

wait for 12 ns;

ZERO_BLANK    <= '0';

VALUE <= "0100";

wait for 12 ns;

ZERO_BLANK <= '0';

VALUE <= "0110";

wait for 7 ns;

end process INPUT_VALUES;

U1: DISPLAY_DECODER

port map(VALUE, ZERO_BLANK, DISPLAY, ZERO_BLANK_OUT);

end ARC_DISPLAY_DECODER_TB;

configuration CFG_DISPLAY_DECODER of DISPLAY_DECODER_TB is

for ARC_DISPLAY_DECODER_TB

for U1:DISPLAY_DECODER use entity

work.DISPLAY_DECODER(BEHAVIOUR);

end for;

end for;

end CFG_DISPLAY_DECODER;
```

